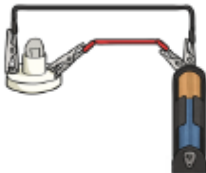
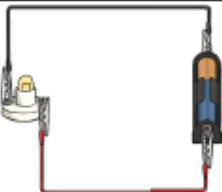

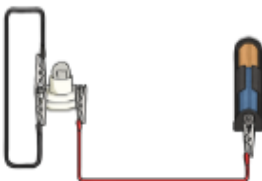


Complete and incomplete circuits

Think about the circuits in the diagrams below; are they complete (bulb will light) or incomplete (bulb will not light)?

| Circuit | Complete or Incomplete? |
|---|-------------------------|
|  | |
|  | |
|  | |
|  | |

What is the difference between the complete and incomplete circuits?